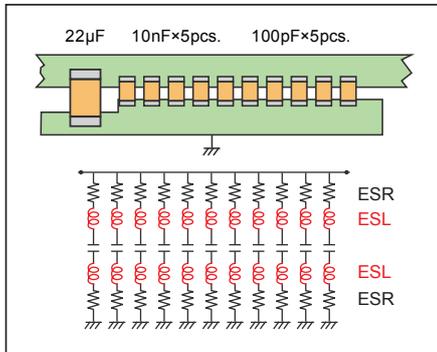


Reducing the Number of Capacitors and Noise by 3-Terminal Capacitors

■ Example <1> MLCC* 11pcs ($22\mu\text{F} + 10\text{nF} \times 5\text{pcs} + 100\text{pF} \times 5\text{pcs}$) → Chip Type 3-Terminal Capacitors $10\mu\text{F}$


*MLCC = Multilayer Ceramic Capacitors

MLCC 11pcs Parallel Connection





Number of Capacitors 1/10

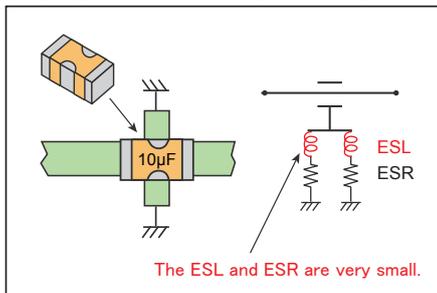Chip Type 3-Terminal Capacitor $10\mu\text{F}$




Insertion Loss

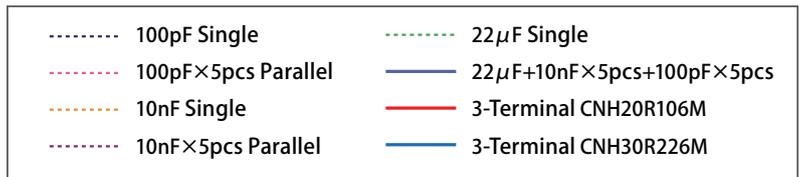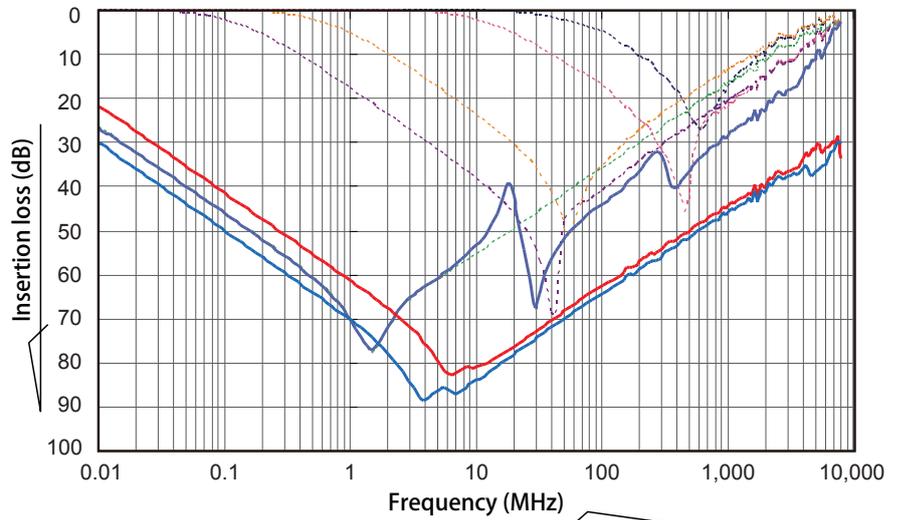


■ Example <2> Tantalum Capacitor $22\mu\text{F}$ + MLCC $0.1\mu\text{F} \times 3\text{pcs}$ → Chip Type 3-Terminal Capacitors $10\mu\text{F}$

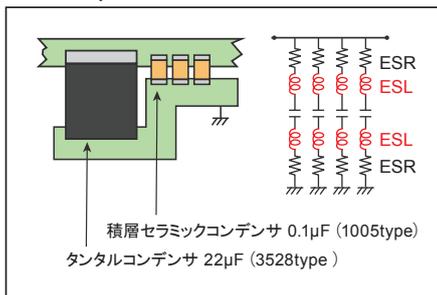Tantalum Capacitor + MLCC 3pcs Parallel Connection



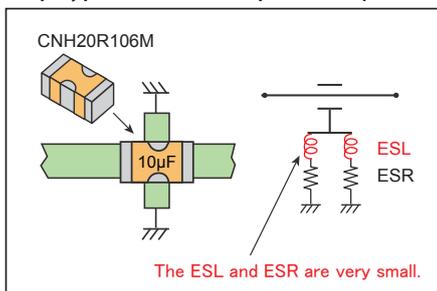Chip Type 3-Terminal Capacitor $10\mu\text{F}$



Insertion Loss

